

DATE:

DETERMINATION OF VOLTAGE IN CIRCUIT

EXP NO: 3

USING NODAL ANALYSIS

AIM:

To determine the voltage in the circuit using nodal analysis both theoretically and practically for a given DC circuit.


APPARATUS REQUIRED:

SNO	APPARATUS	SPECIFICATION	QUANTITY
1	Regulated Power Supply	(0-30)V	1
2	Multimeter		1
3	Resistor	470 Ω , 330 Ω	3, 2
4	Bread board	-	1

PROCEDURE:

1. Give connections as per the circuit diagram.
2. Switch ON the supply, vary the RPS and set a particular input voltage.
3. Note down the readings of ammeters and voltmeters and tabulate them.
4. Vary the RPS to its minimum value and switch off the supply.
5. Reduce the RPS to its minimum value and switch off the supply.
6. Using the tabulated values, verify Kirchhoff's laws practically and verify it theoretically.

CIRCUIT DIAGRAM:

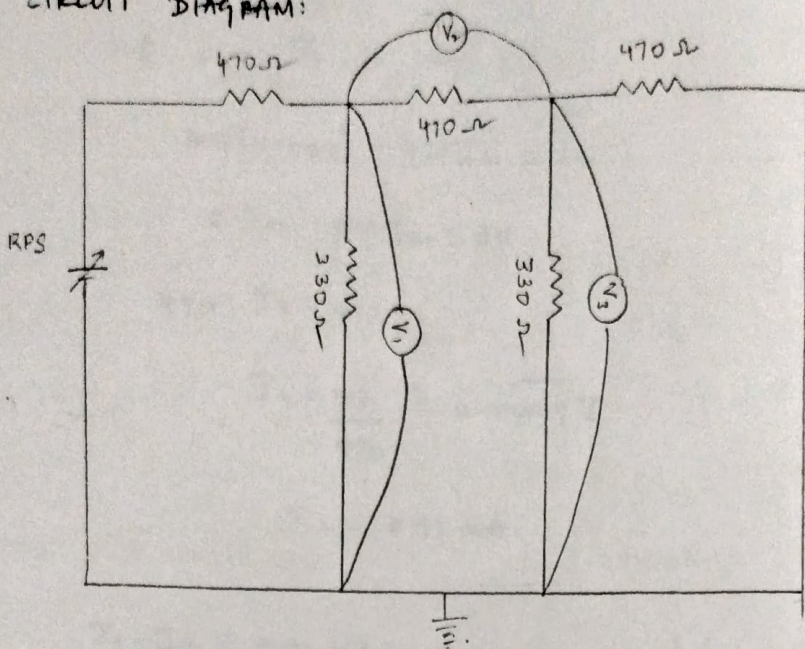

TABULAR COLUMN:

PARAMETERS	THEORETICAL	PRACTICAL
I_1	0.688V	0.69V
I_2	0.452V	0.48V
$I_1 - I_2$	0.186V	0.19V

CALCULATION:

Let D point be ground $\rightarrow V_D = 0$

Let potential at points A and B be V_A and V_B using nodal analysis at node A,

current entering = 0

$$\text{current leaving} = \frac{V_A}{330} + \frac{V_A - V_B}{470} + \frac{V_A - 2}{470}$$

By KCL,
$$\frac{V_A}{330} + \frac{V_A - V_B}{470} + \frac{V_A - 2}{470} = 0$$

$$2 \frac{V_A - V_B - 2}{470} + \frac{V_A}{330} = 0$$

RESULT:

Thus, The nodal analysis verified practically and theoretically. The resultant voltage for 2V supply are:

- a) The voltage V_1 is 0.632 V
- b) The voltage V_2 is 0.186 V
- c) The voltage V_3 is 0.452 V .

$$330 (2V_A - V_B - 2) + 470 V_A = 0$$

$$660 V_A - 330 V_B - 660 + 470 V_A = 0$$

$$1130 V_A - 330 V_B = 660 \quad \text{--- (1)}$$

At node B:

current entering = 0

$$\text{current leaving} = \frac{V_B - V_A}{470} + \frac{V_B}{470} + \frac{V_B}{330}$$

By KCL,

$$\frac{V_B - V_A}{470} + \frac{V_B}{470} + \frac{V_B}{330} = 0$$

$$330 (2V_B - V_A) + 470 V_B = 0$$

$$660 V_B - 330 V_A + 470 V_B = 0$$

$$-330 V_A + 1130 V_B = 0 \quad \text{--- (2)}$$

Solving (1) and (2).

$$V_A = 0.638 \text{ V} = V_1$$

$$V_B = 0.186 \text{ V} = V_3$$

$$V_2 = V_A - V_B = 0.638 - 0.186 \\ = 0.452 \text{ V}$$